

BJT AC Analysis



Topic 5 (Chapter 5)

AC Amplification

- After a transistor has been biased with the Q point near the middle of the load line, we can couple a small ac voltage into the base.
 - This will produce an ac collector voltage.
 - The ac collector voltage looks like the ac base voltage, except that it's a lot bigger.
 - In other words, the ac collector voltage is an *amplified* version of the ac base voltage.
- The invention of amplifying devices, first vacuum tubes and later transistors, was crucial to the evolution of electronics.
 - Without amplification, there would be no radio, no television, and no computers.

BJT amplifier biased at a point Q

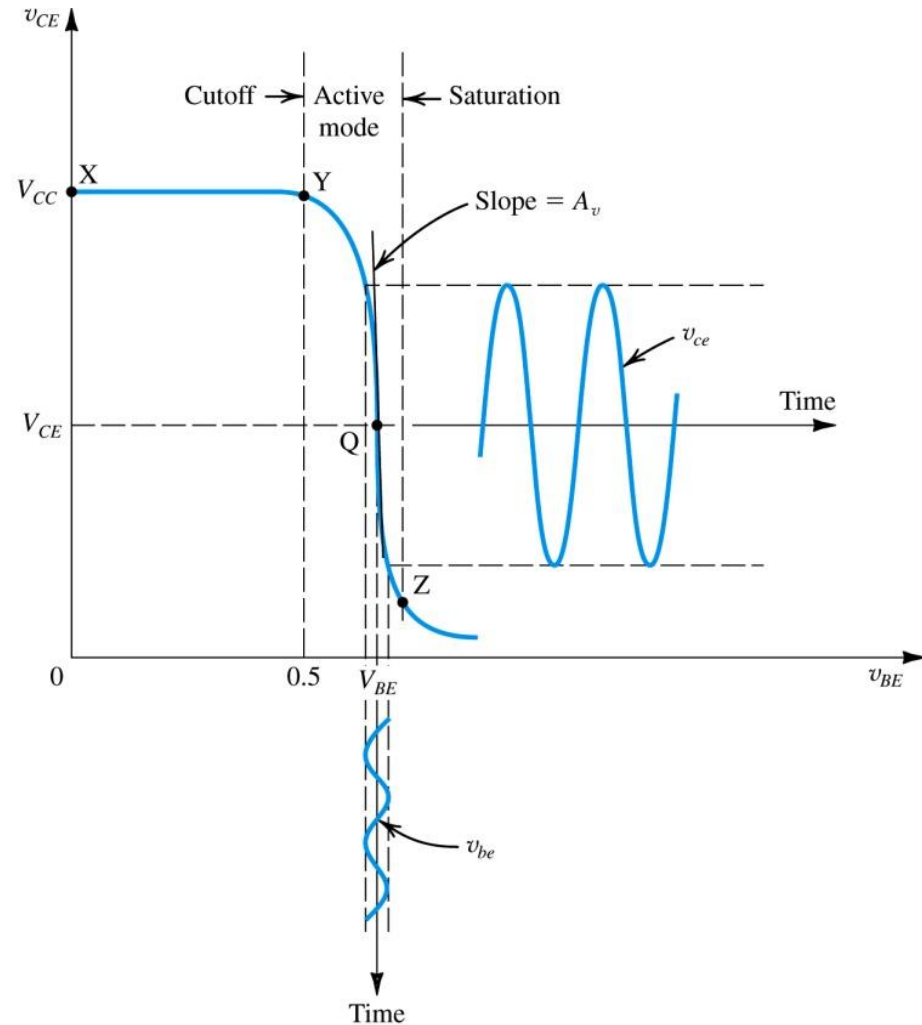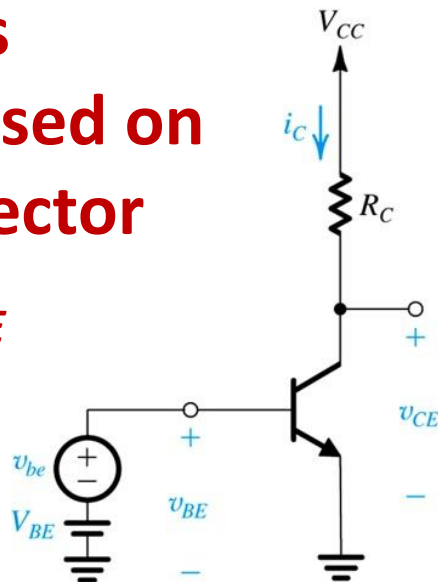- A small signal voltage v_{be} is applied
- The output signal v_{ce} appears superimposed on the dc collector voltage V_{CE}




- The amplitude of v_{ce} is larger than that of v_{be} by the voltage gain A_v

Base-biased amplifier

- **AC** input is applied into base
- Coupling capacitors are used to block DC
 - The **reactance** of a coupling capacitor is small for AC signal
- Amplified and inverted **output** at the collector
- **AC** output coupled to the load


A base-biased amplifier with capacitive coupling

Coupling capacitors are used to block DC

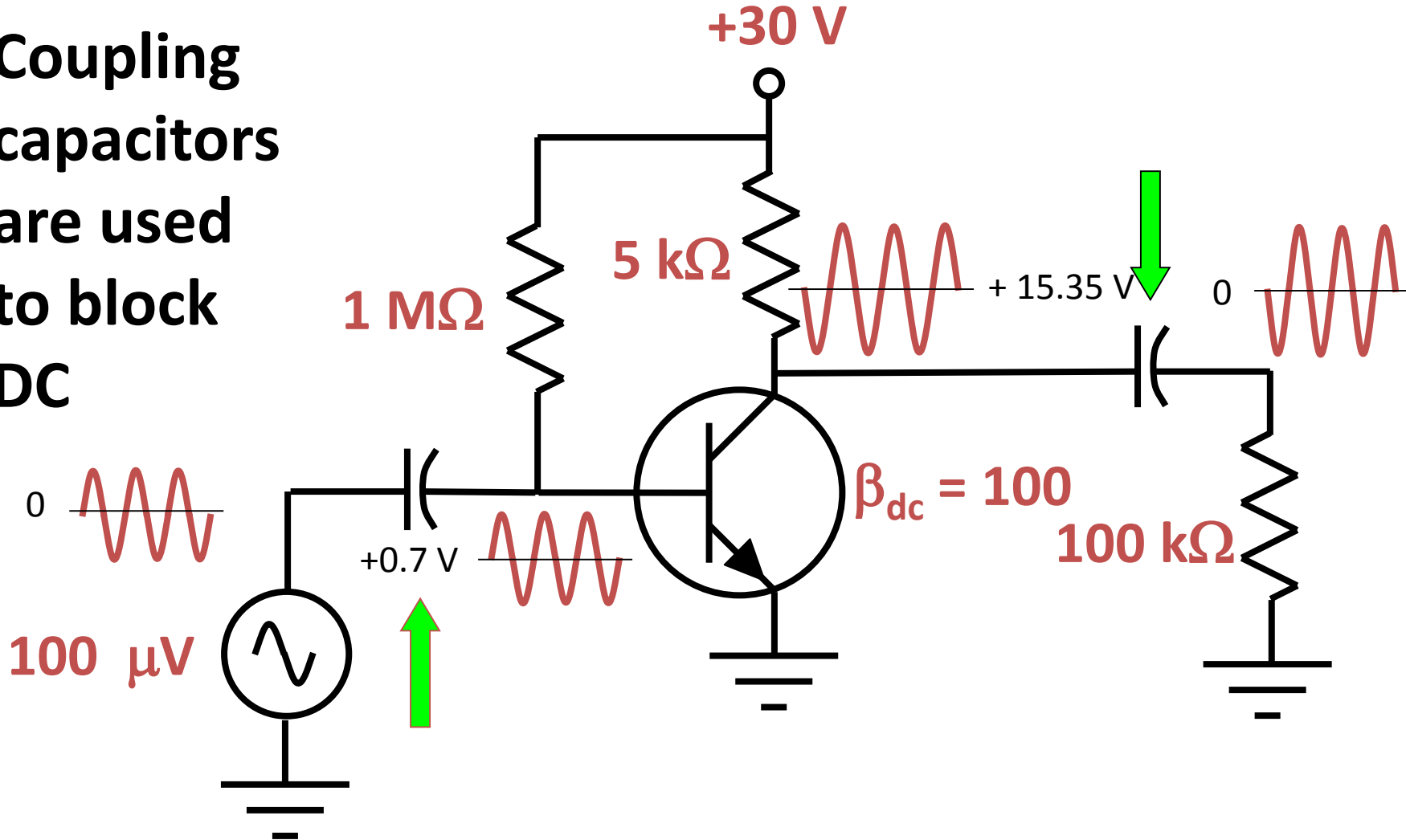


DC analysis gives: $I_B = 29.3\ \mu\text{A}$, $I_C = 2.93\ \text{mA}$ and $V_C = 15.35\ \text{V}$

Current Waveforms

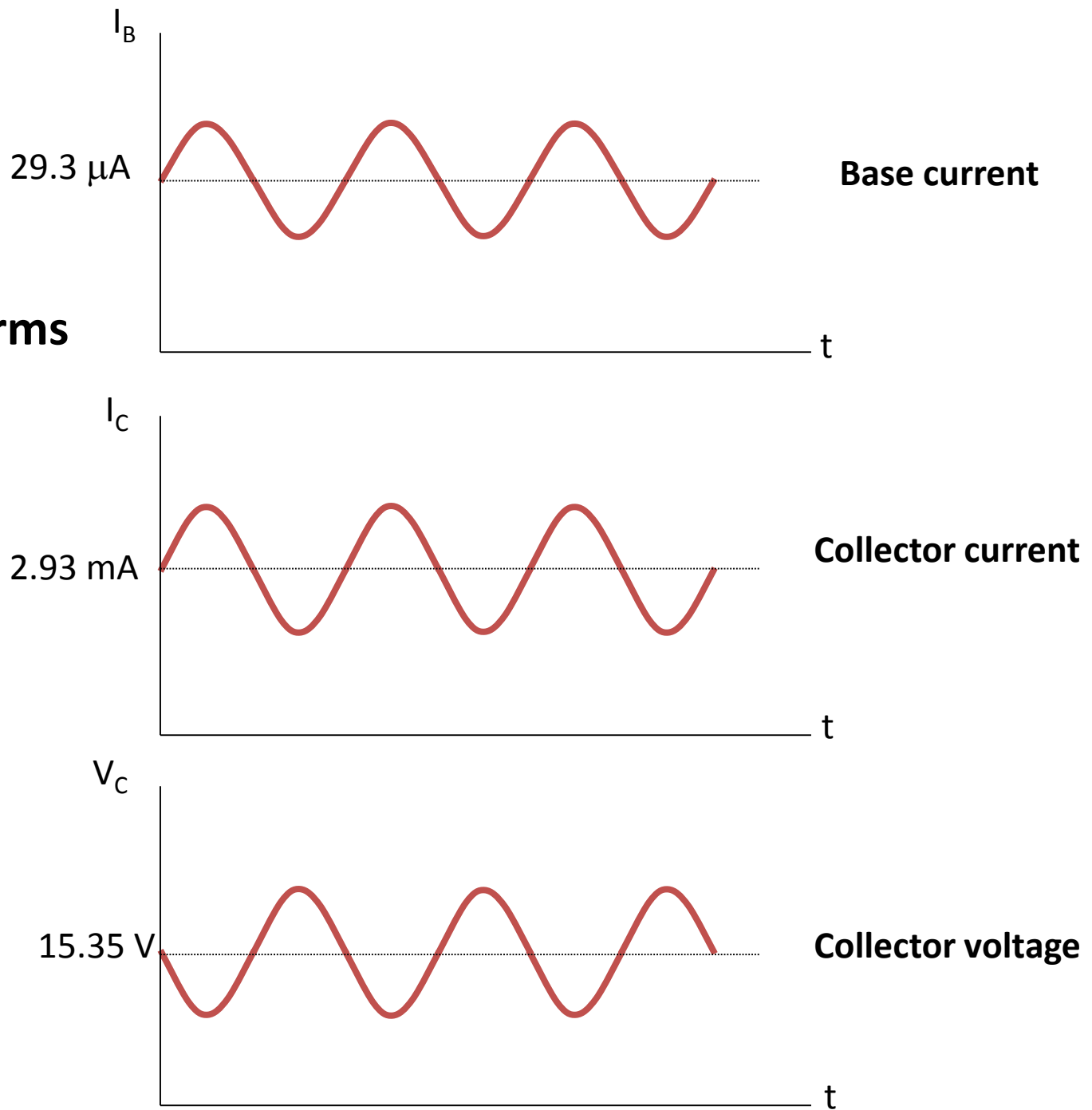

The coupling capacitor

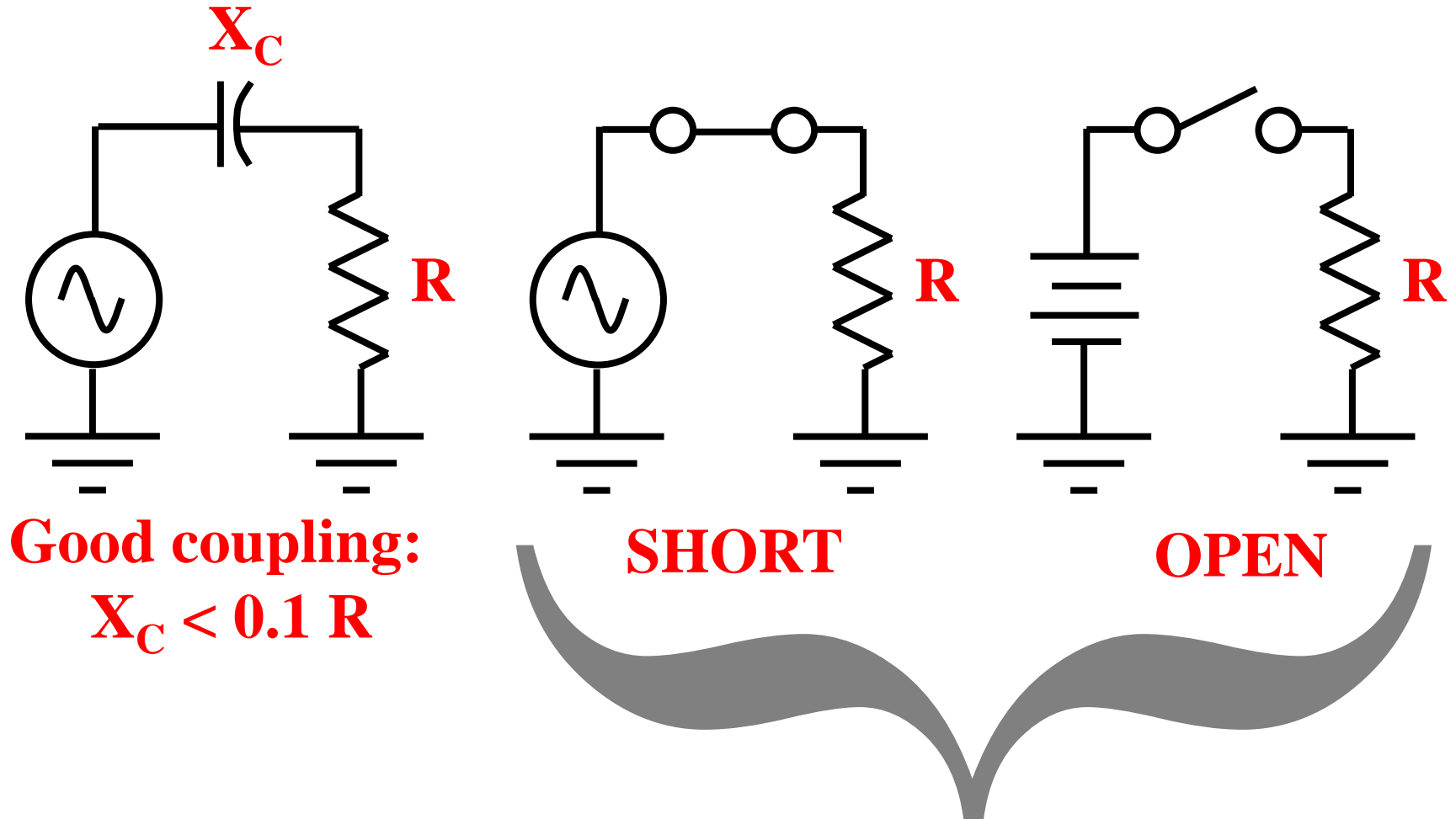


1. For **ac** analysis, the capacitor is a **short**.
2. For **dc** analysis, the capacitor is **open**.

VDB Amplifier


- **Dc** voltages and currents are calculated mentally by opening capacitors
- The **ac** signal is coupled via a coupling capacitor
- The **bypass** capacitor causes an ac signal to appear across the base-emitter junction and provides higher gain

VDB Amplifier

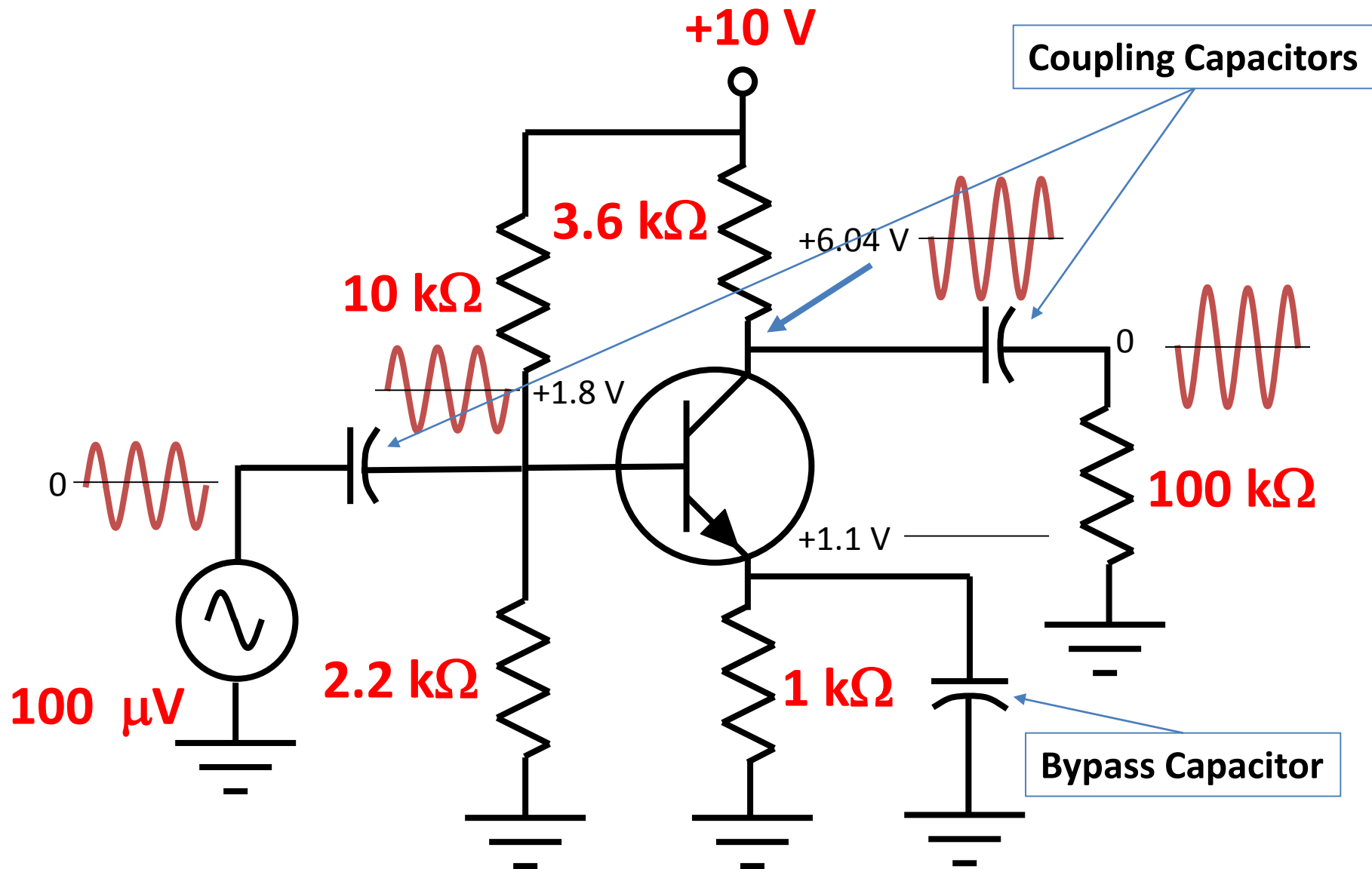

Distortion

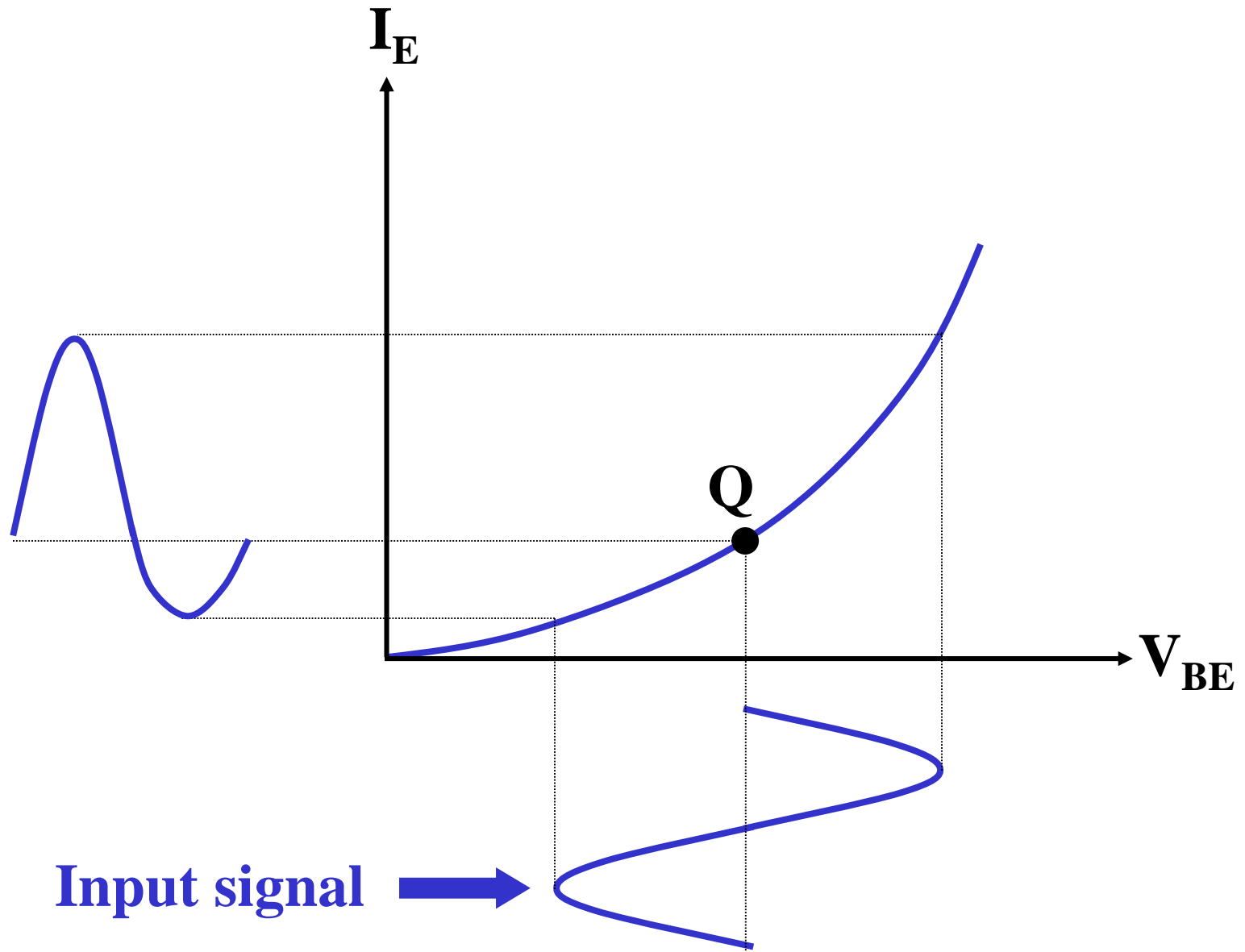
- The **stretching and compressing** of alternate half cycles
- **Undesirable** in high-fidelity amplifiers
- Can be **minimized** by keeping the ac input small



Large-signal operation produces distortion

The 10 percent rule

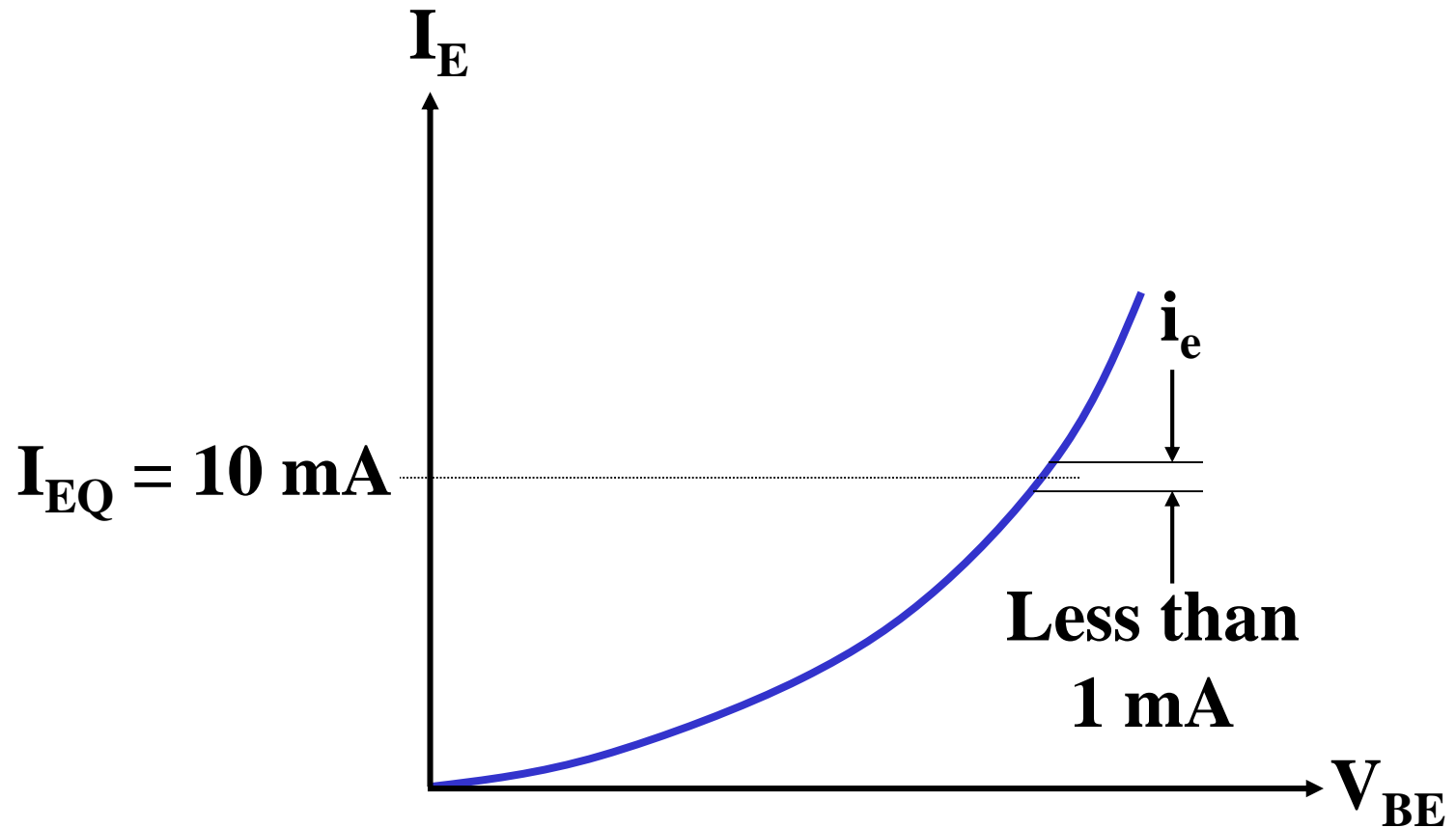- Total **emitter current** consists of dc and ac
- To **minimize** distortion, i_e must be small compared to I_{EQ}
- The **ac** signal is small when the peak-to-peak ac emitter current is less than **10 percent** of the dc emitter current



Total emitter current: $I_E = I_{EQ} + i_e$

Small-signal operation: $i_{e(\text{PP})} < 0.1 I_{EQ}$


The dc current gain is given as:

$$\beta_{dc} = \frac{I_C}{I_B}$$

The ac current gain is given as:

$$\beta_{ac} = \frac{i_c}{i_b}$$

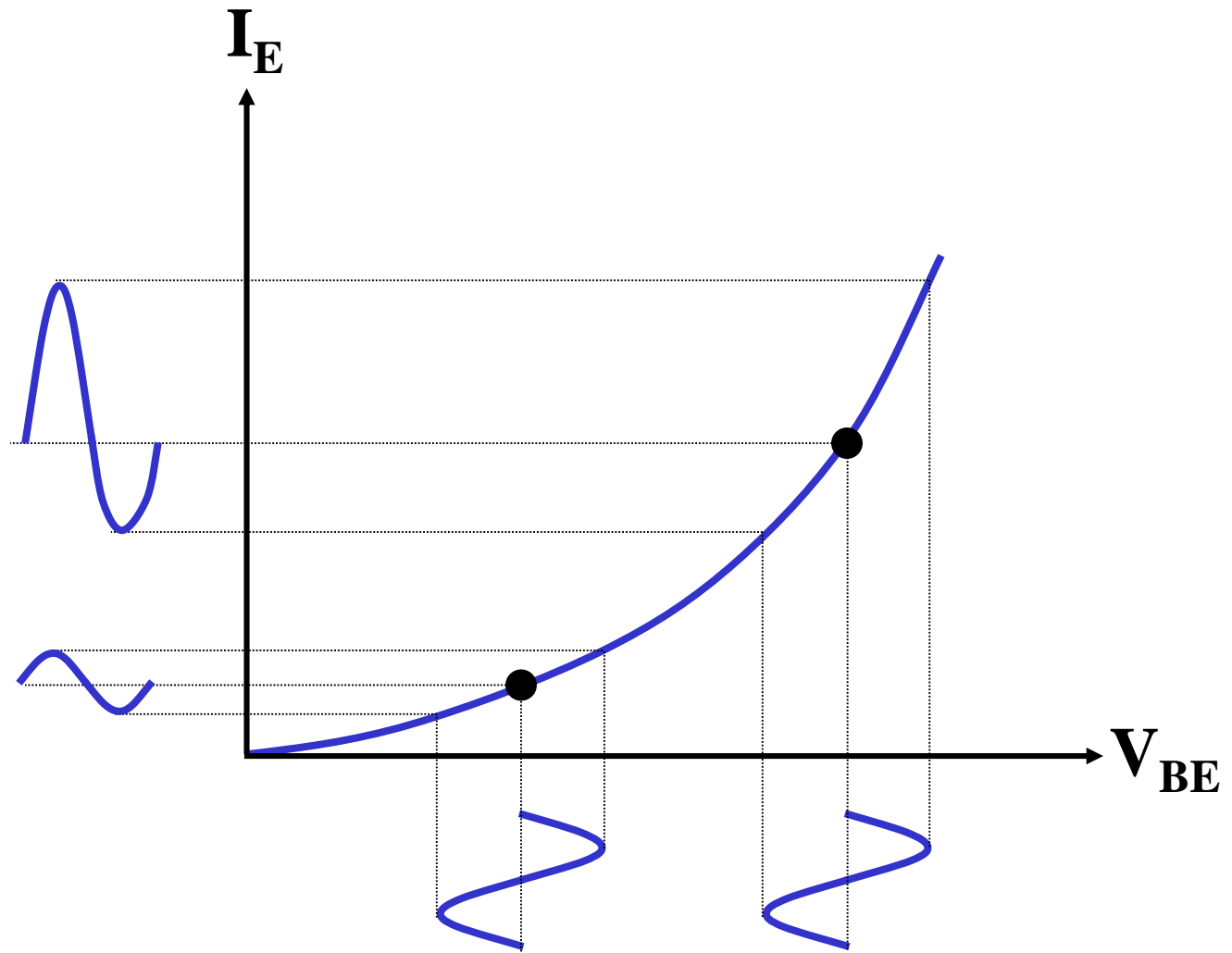Use **CAPITAL** letters for dc quantities
and **lowercase** letters for ac.



The size of the ac emitter current depends on the Q point.

Total emitter current: $I_E = I_{EQ} + i_e$

Total base-emitter voltage: $V_{BE} = V_{BEQ} + v_{be}$


The ac resistance of the emitter diode is defined as:

$$r_e' = \frac{v_{be}}{i_e}$$

The ac resistance of the emitter diode decreases when the **dc** emitter current increases

Ac resistance of the emitter diode

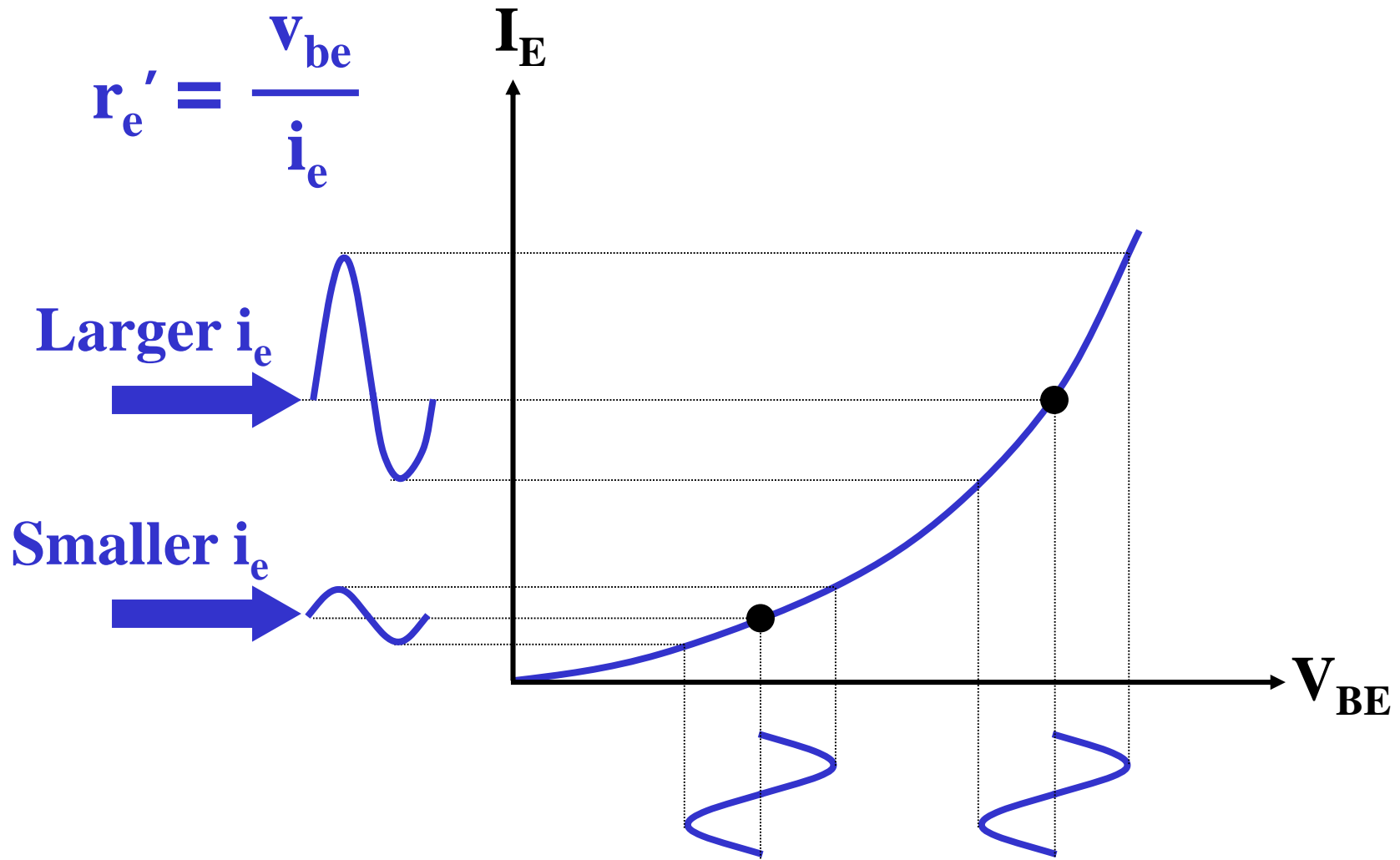- Equals the **ac** base-emitter voltage divided by the **ac** emitter current
- The prime (') in r_e' indicates that the **resistance** is inside the transistor



Note that r_e' varies with the operating point.

This implies that r_e' is a function of the dc emitter current.

Formula for ac emitter resistance


**Derived by using solid-state physics
and calculus:**

$$r_e' = \frac{26 \text{ mV}}{I_E}$$

**Widely used in industry because of its
simplicity and it applies to almost all
commercial transistors**

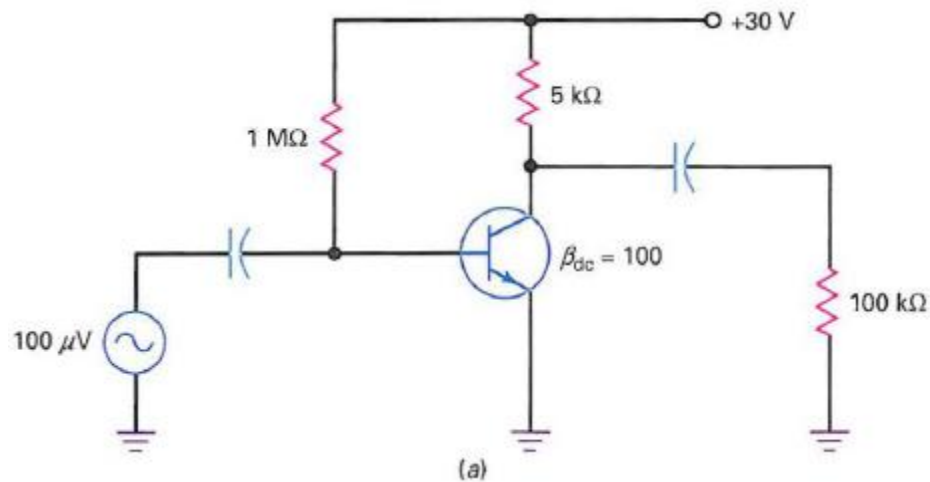Example 9-4


What does r'_e equal in the base-biased amplifier of Fig. 9-15a?



$$r'_e = \frac{25 \text{ mV}}{3 \text{ mA}} = 8.33 \, \Omega$$

Example 9-5




In Fig. 9-15*b*, what does r'_e equal?

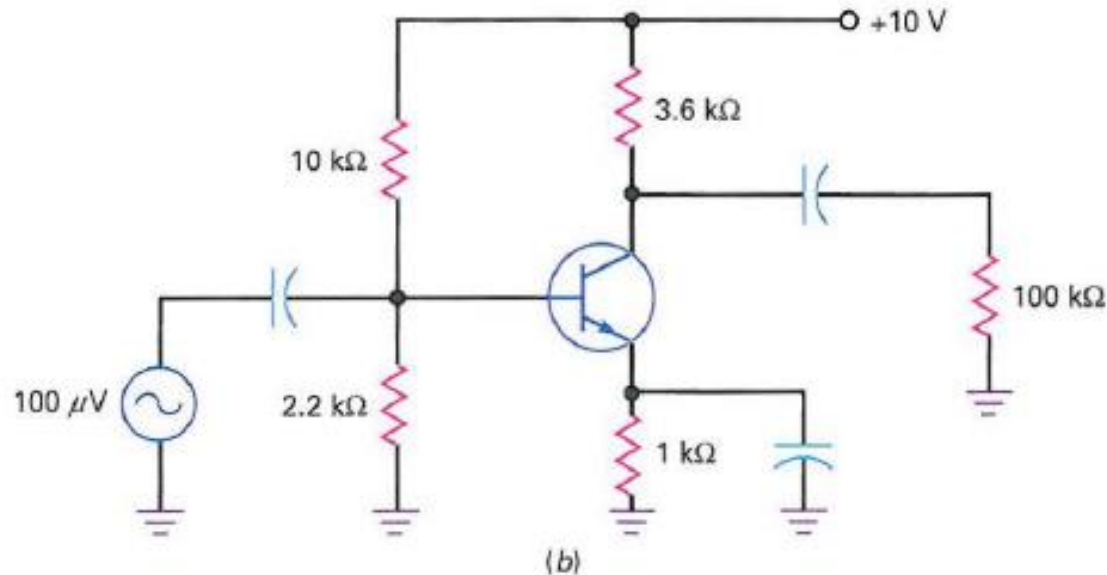

SOLUTION We analyzed this VDB amplifier earlier and calculated a dc emitter current of 1.1 mA. The ac resistance of the emitter diode is:

$$r'_e = \frac{25 \text{ mV}}{1.1 \text{ mA}} = 22.7 \, \Omega$$

BJT TRANSISTOR MODELING

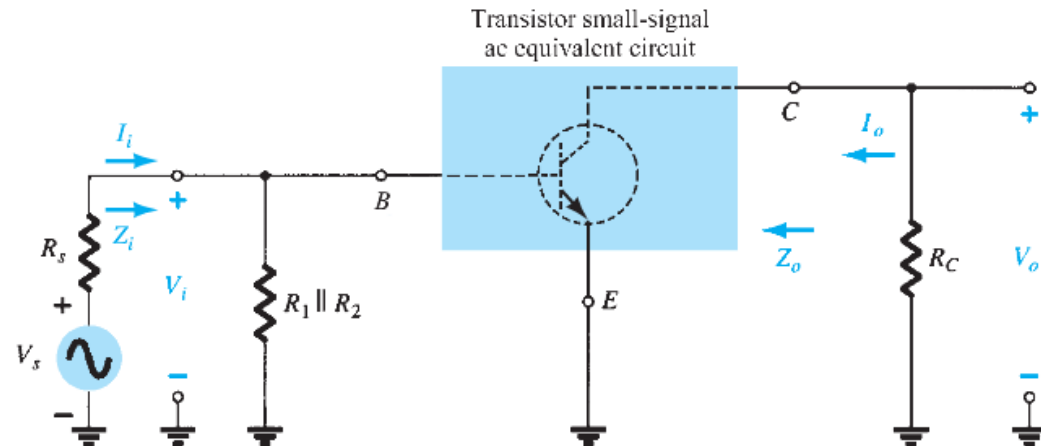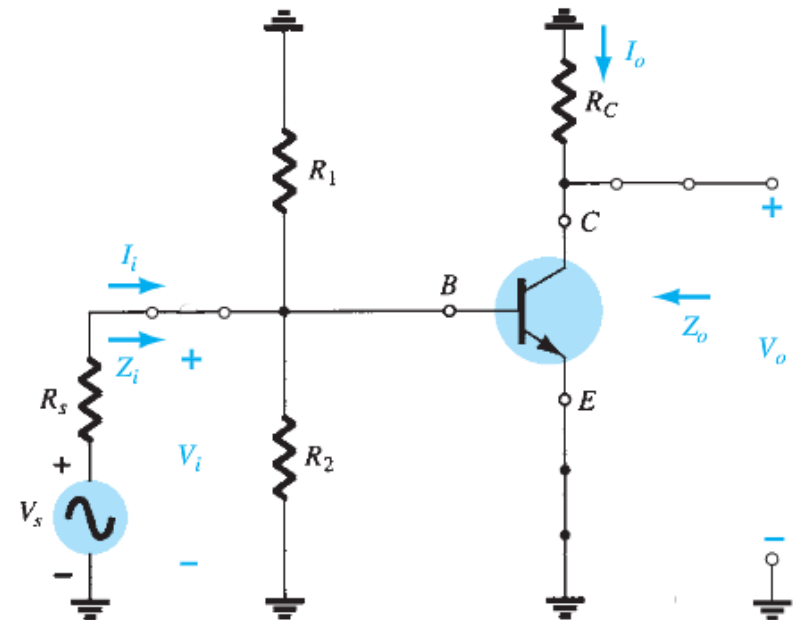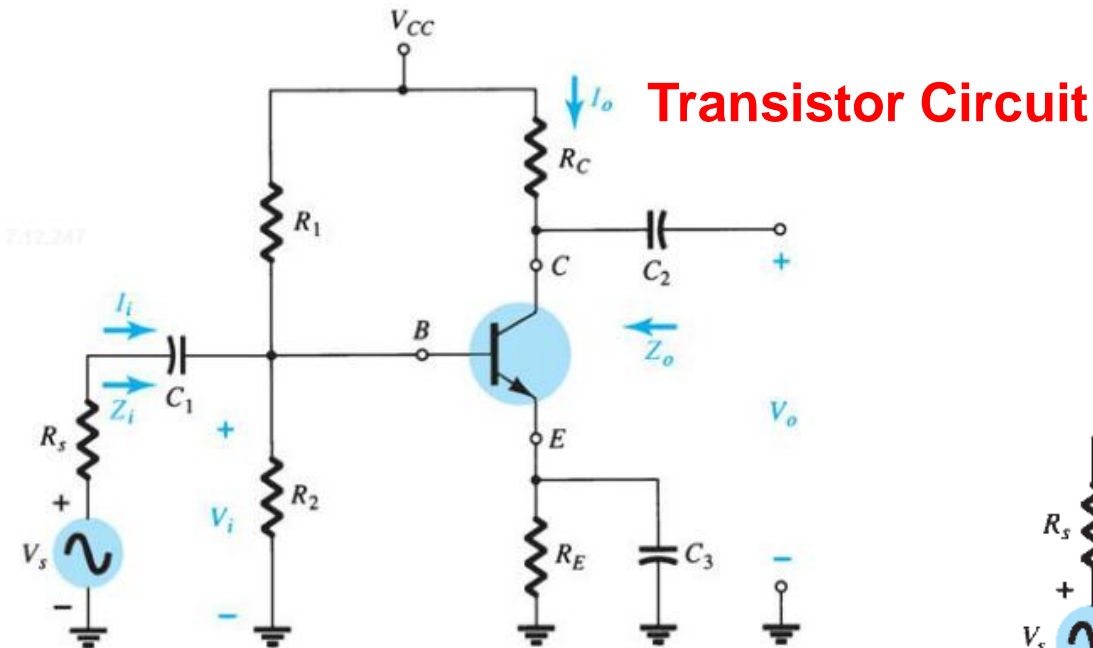

AC Equivalent Circuit:
After the removal of the dc supply and insertion of the short-circuit equivalent for the capacitors.

Redrawn for small-signal ac analysis

Transistor models

- **Ac equivalent** circuit for a transistor
- **Simulates** how a transistor behaves when an ac signal is present
- There are two models commonly used in small signal AC analysis of a transistor:
 - **r_e model**
 - **Ebers-Moll** (T model) and **π** type models are widely used
 - **Hybrid equivalent model (h parameter model)**

The r_e Transistor Model

(The Input Equivalent Circuit)

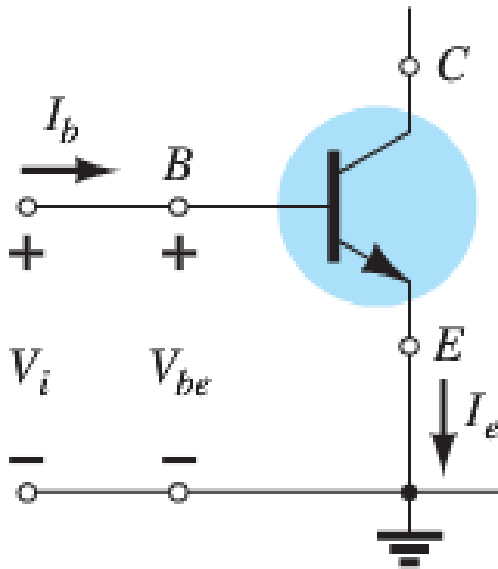


FIG. 5.8

Finding the input equivalent circuit for a BJT transistor.

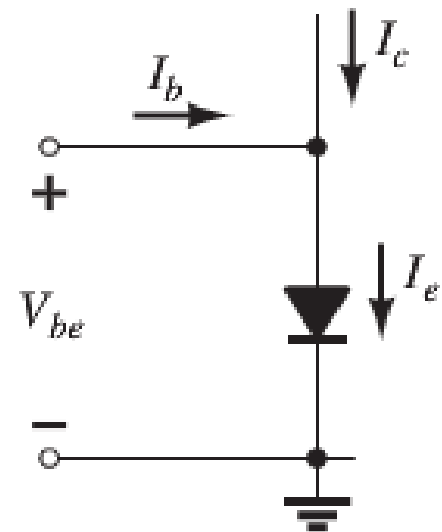


FIG. 5.10

Equivalent circuit for the input side of a BJT transistor.

The r_e Transistor Model

(The BJT Equivalent Circuit – T Model)

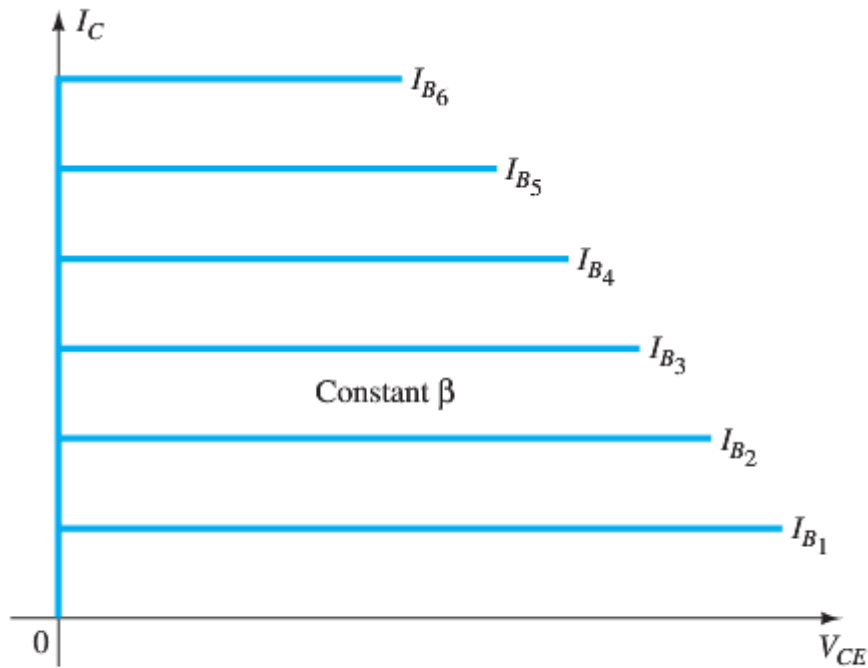


FIG. 5.11

Constant β characteristics.

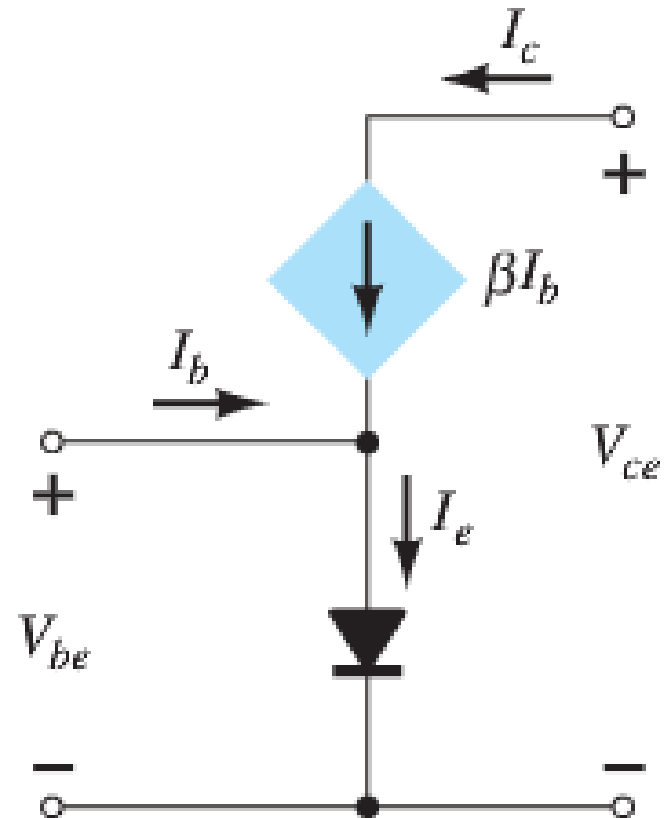


FIG. 5.12

BJT equivalent circuit.

The T model of a transistor:


$$V_{be} = i_e r_e'$$

$$Z_{in(base)} = \frac{V_{be}}{i_b}$$


$$= \frac{i_e r_e'}{i_b}$$

$$= (\beta + 1) r_e'$$

$$\approx \beta r_e'$$

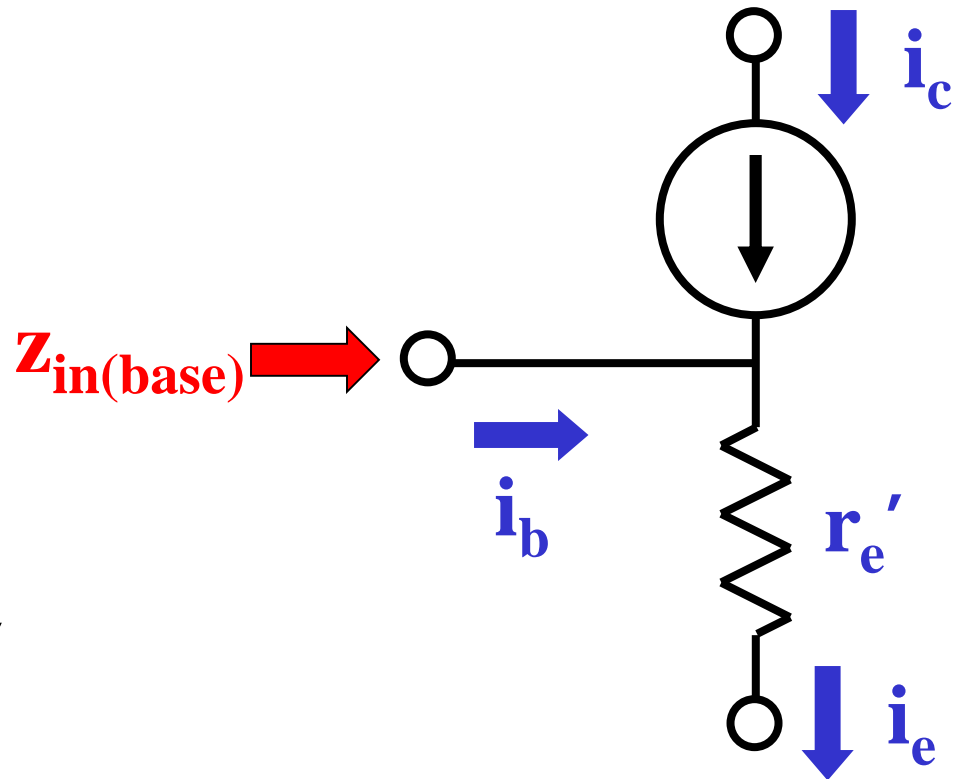

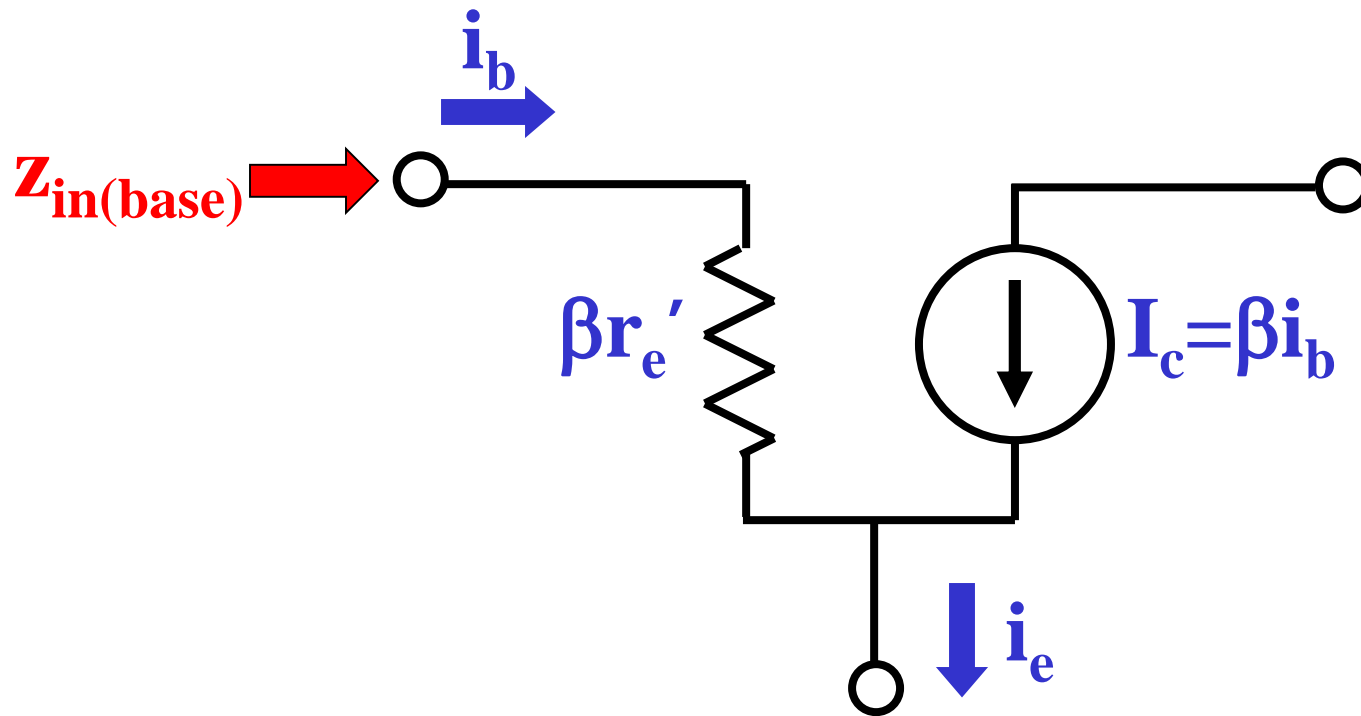The π model of a transistor
is based on $z_{in(base)} = \beta r_e'$:



Clearly shows the **input impedance of $\beta r_e'$** will load the ac voltage source driving the base

Overview of r_e Transistor Models

(T and π Model)



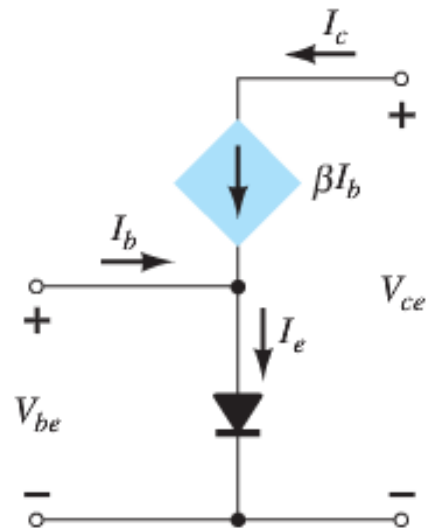


FIG. 5.12
BJT equivalent circuit.

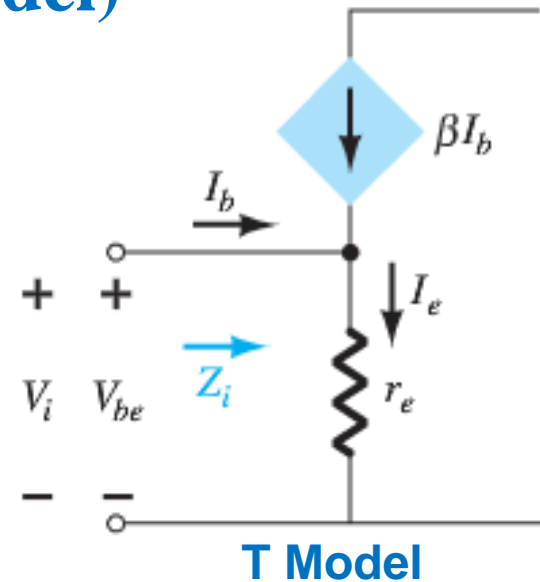


T Model

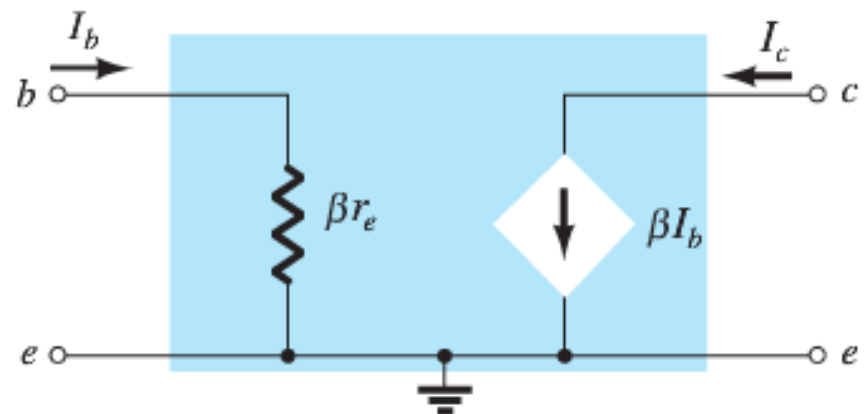

π Model

Early voltage and modeling the output impedance

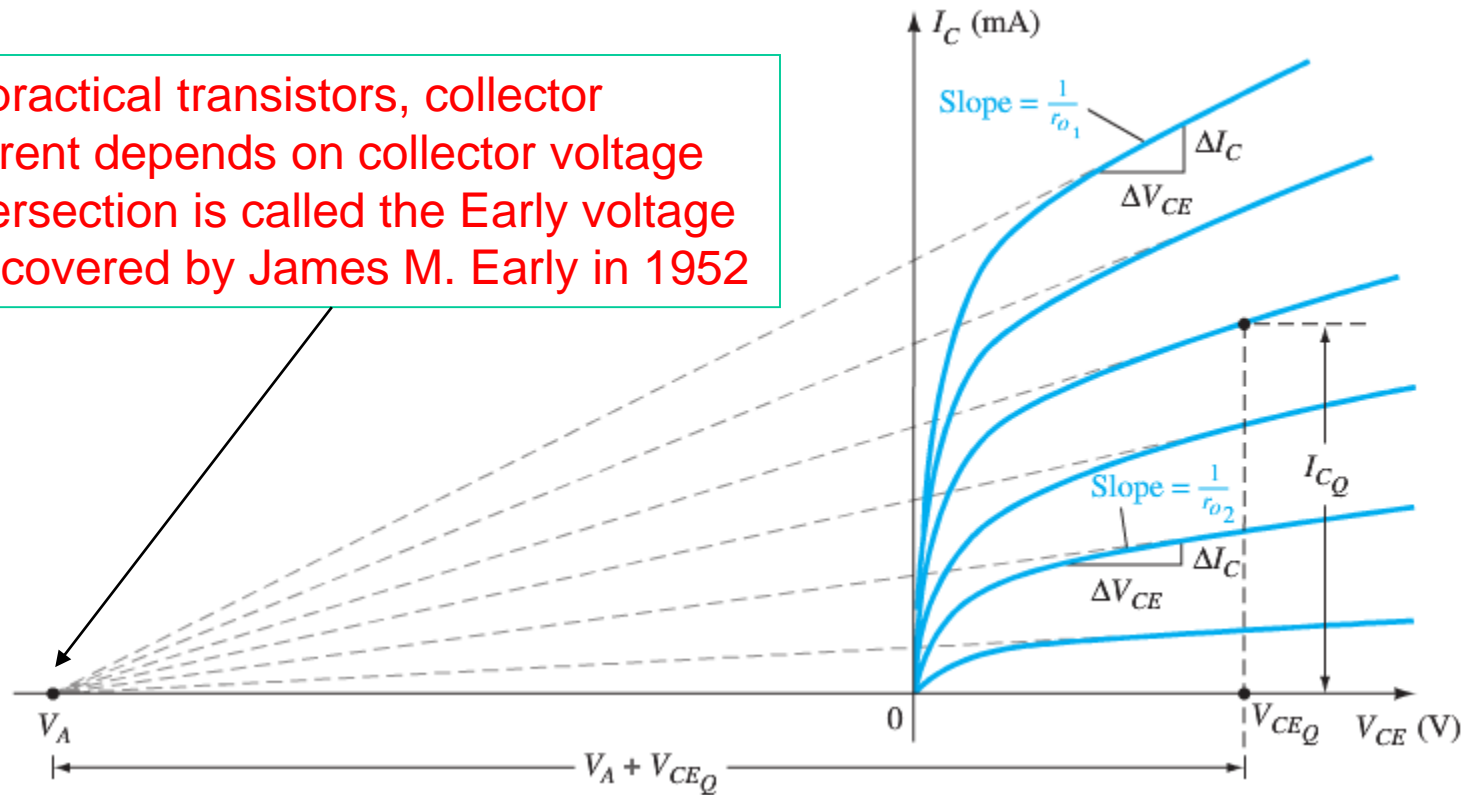- In practical transistors, collector current depends on collector voltage
- Intersection is called the Early voltage
- Discovered by James M. Early in 1952



$$r_o = \frac{\Delta V}{\Delta I} = \frac{V_A + V_{CEQ}}{I_{CQ}}$$


$$r_o \cong \frac{V_A}{I_{CQ}}$$

If Early voltage is not available,

$$\text{Slope} = \frac{\Delta y}{\Delta x} = \frac{\Delta I_C}{\Delta V_{CE}} = \frac{1}{r_o}$$

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}$$



r_e model including effects of r_o

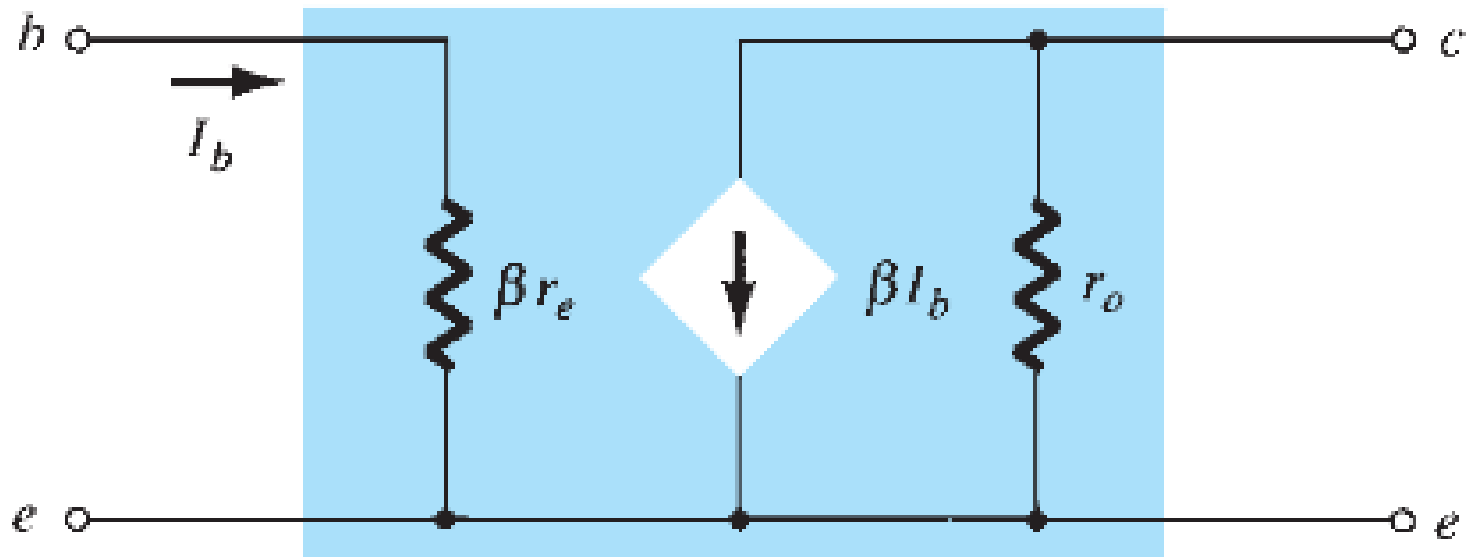

Reasons for Slight Upward Slope of Collector Curves

- CB depletion layer widens with increasing V_{CE}
 - Narrows the base
 - Fewer holes available for recombination
- Results in smaller I_B and higher I_C

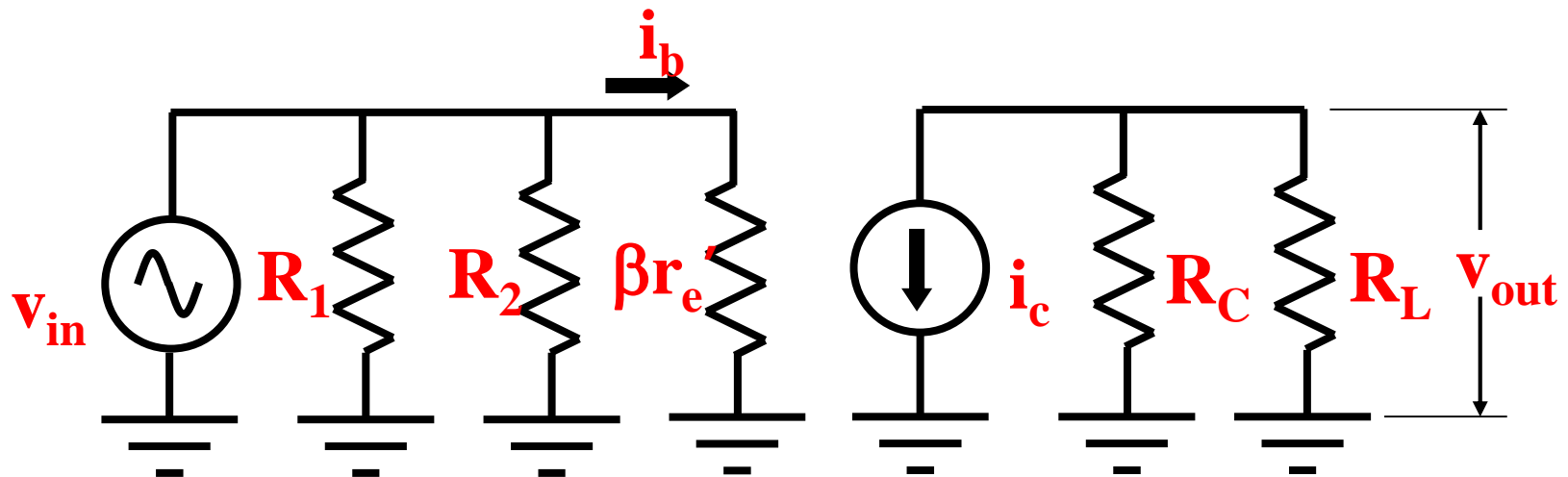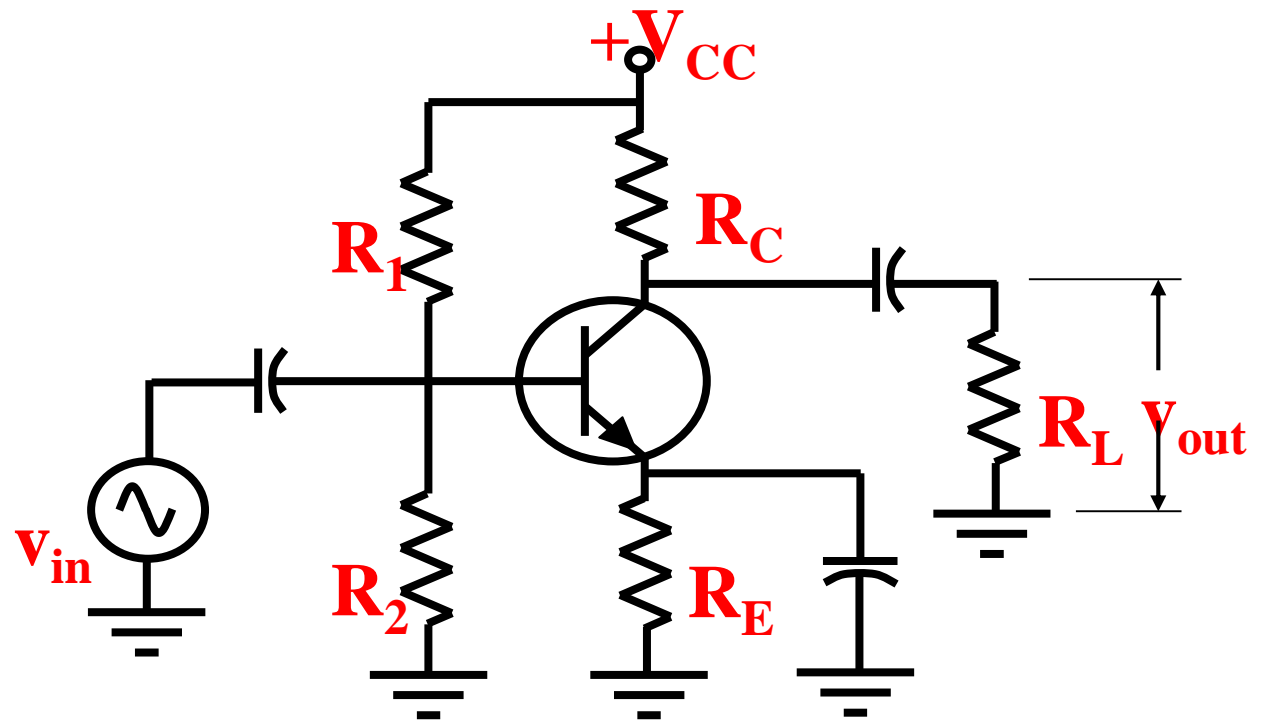π model of
the VDB
common-
emitter
amplifier





This model best illustrates that $z_{in(stage)} = R_1 \parallel R_2 \parallel \beta r_e'$


Amplifier analysis

- **Perform** a complete dc analysis
- **Mentally** short all coupling and bypass capacitors for ac signals
- **Visualize** all dc supply voltages as ac grounds
- **Replace** the transistor by its π or T model
- **Draw** the ac equivalent circuit

Common-Emitter Fixed-Bias Configuration

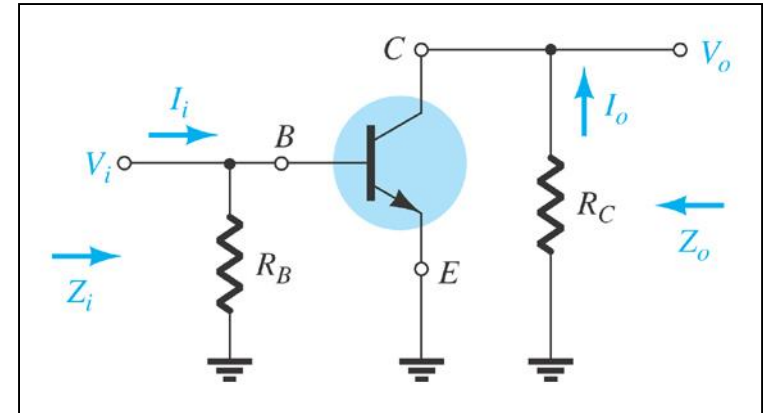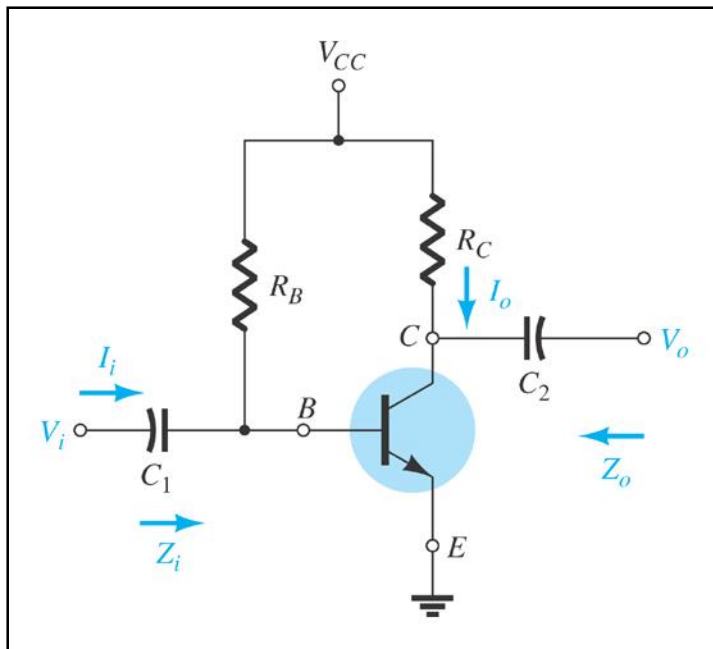

AC equivalent

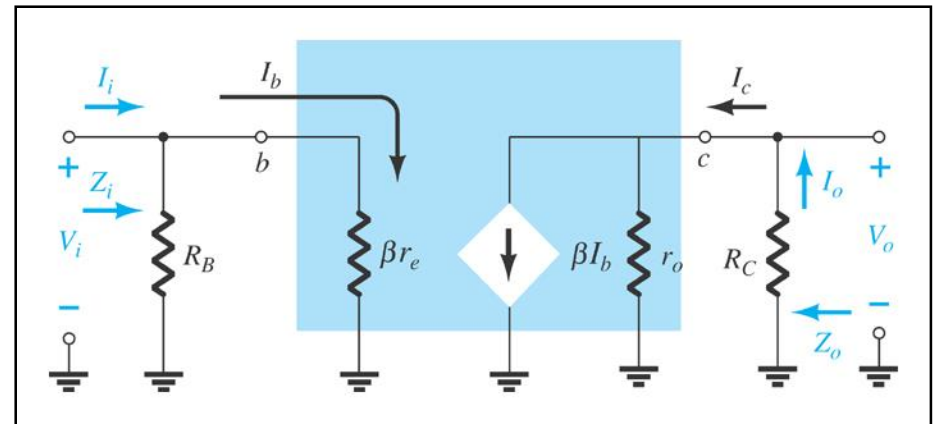

r_e model

Common-Emitter Fixed-Bias Calculations

Input
impedance:

$$Z_i = R_B \parallel \beta r_e$$

$$Z_i \cong \beta r_e \mid_{R_E \geq 10\beta r_e}$$

Output
impedance:


$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \mid_{r_o \geq 10R_C}$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$
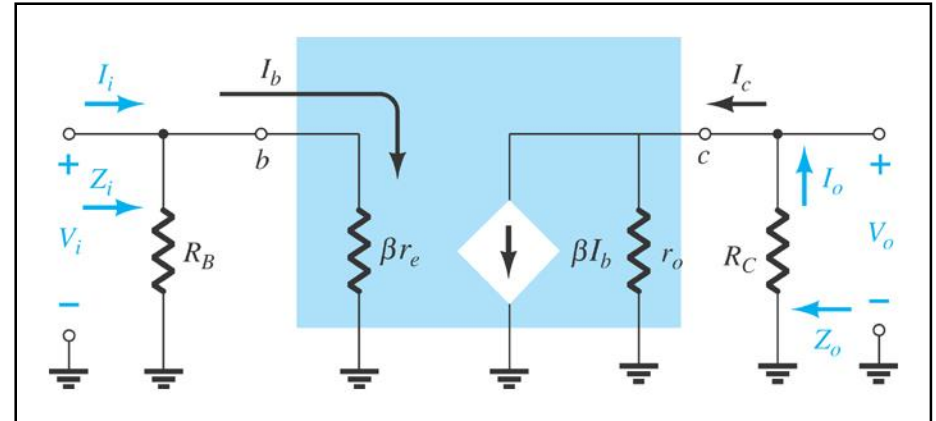
$$A_v = -\frac{R_C}{r_e} \mid_{r_o \geq 10R_C}$$



Current gain:

$$A_i = \frac{I_o}{I_i} = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)}$$

$$A_i \cong \beta \mid_{r_o \geq 10R_C, R_B \geq 10\beta r_e}$$

Current gain
from voltage gain:

$$A_i = -A_v \frac{Z_i}{R_C}$$

EXAMPLE 5.1 For the network of Fig. 5.25:

- Determine r_e .
- Find Z_i (with $r_o = \infty \Omega$).
- Calculate Z_o (with $r_o = \infty \Omega$).
- Determine A_v (with $r_o = \infty \Omega$).
- Repeat parts (c) and (d) including $r_o = 50 \text{ k}\Omega$ in all calculations and compare results.

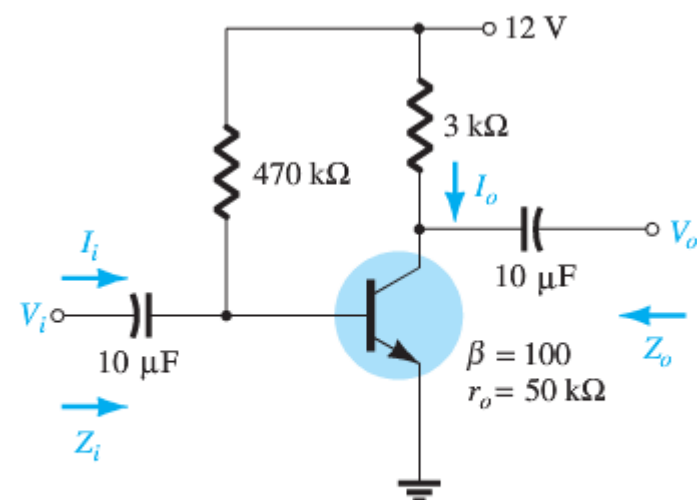


FIG. 5.25

Example 5.1.

Solution:

a. DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = 24.04 \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (101)(24.04 \mu\text{A}) = 2.428 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.428 \text{ mA}} = \mathbf{10.71 \Omega}$$

b. $\beta r_e = (100)(10.71 \Omega) = 1.071 \text{ k}\Omega$

$$Z_i = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel 1.071 \text{ k}\Omega = \mathbf{1.07 \text{ k}\Omega}$$


c. $Z_o = R_C = \mathbf{3 \text{ k}\Omega}$

d. $A_v = -\frac{R_C}{r_e} = -\frac{3 \text{ k}\Omega}{10.71 \Omega} = \mathbf{-280.11}$


e. $Z_o = r_o \parallel R_C = 50 \text{ k}\Omega \parallel 3 \text{ k}\Omega = \mathbf{2.83 \text{ k}\Omega}$ vs. $3 \text{ k}\Omega$

$$A_v = -\frac{r_o \parallel R_C}{r_e} = \frac{2.83 \text{ k}\Omega}{10.71 \Omega} = \mathbf{-264.24}$$
 vs. -280.11

Common-Emitter Voltage-Divider Bias

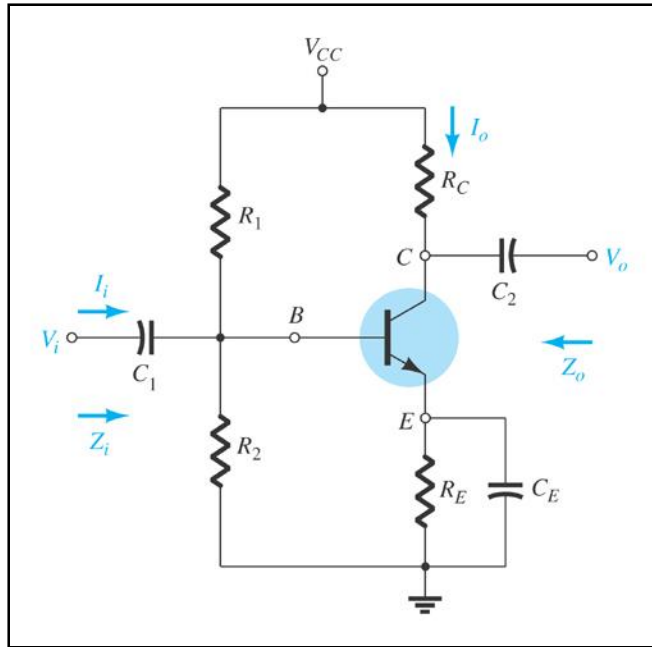

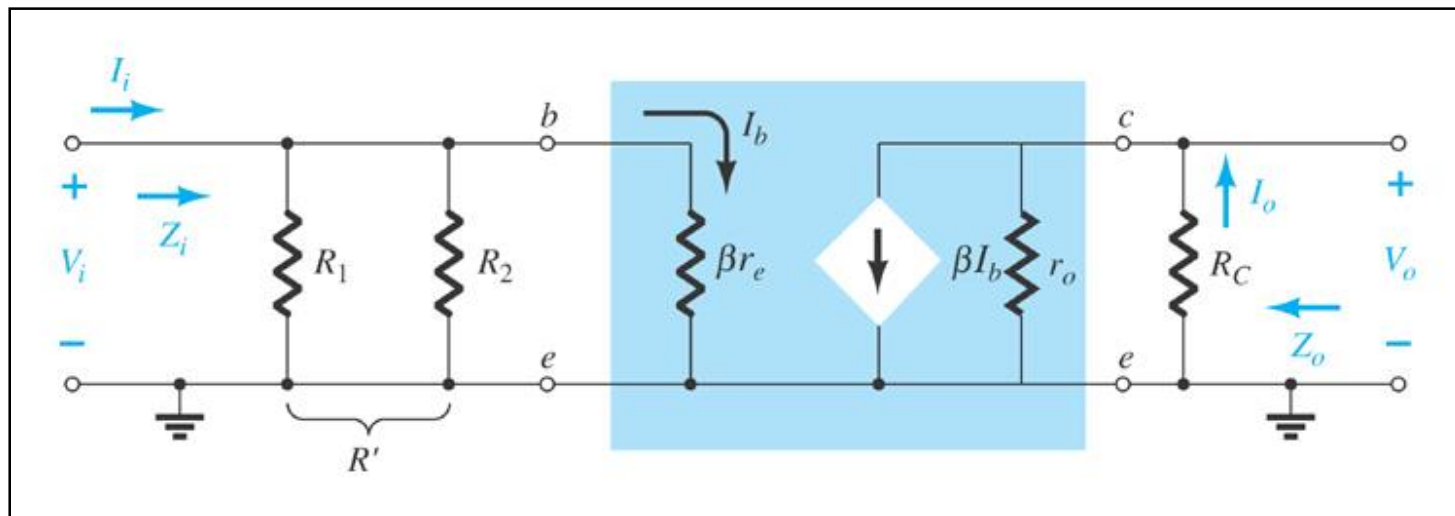r_e model requires you to determine β , r_e , and r_o .



Common-Emitter Voltage-Divider Bias

Input impedance

$$R' = R_1 \parallel R_2$$

$$Z_i = R' \parallel \beta r_e$$

Output impedance

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \big|_{r_o \geq 10R_C}$$

Voltage gain

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e} \big|_{r_o \geq 10R_C}$$

Current gain


$$A_i = \frac{I_o}{I_i} = \frac{\beta R' r_o}{(r_o + R_C)(R' + \beta r_e)}$$

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R'}{R' + \beta r_e} \big|_{r_o \geq 10R_C}$$

$$A_i = \frac{I_o}{I_i} \cong \beta \big|_{r_o \geq 10R_C, R' \geq 10\beta r_e}$$

Current gain from A_v

$$A_i = -A_v \frac{Z_i}{R_C}$$

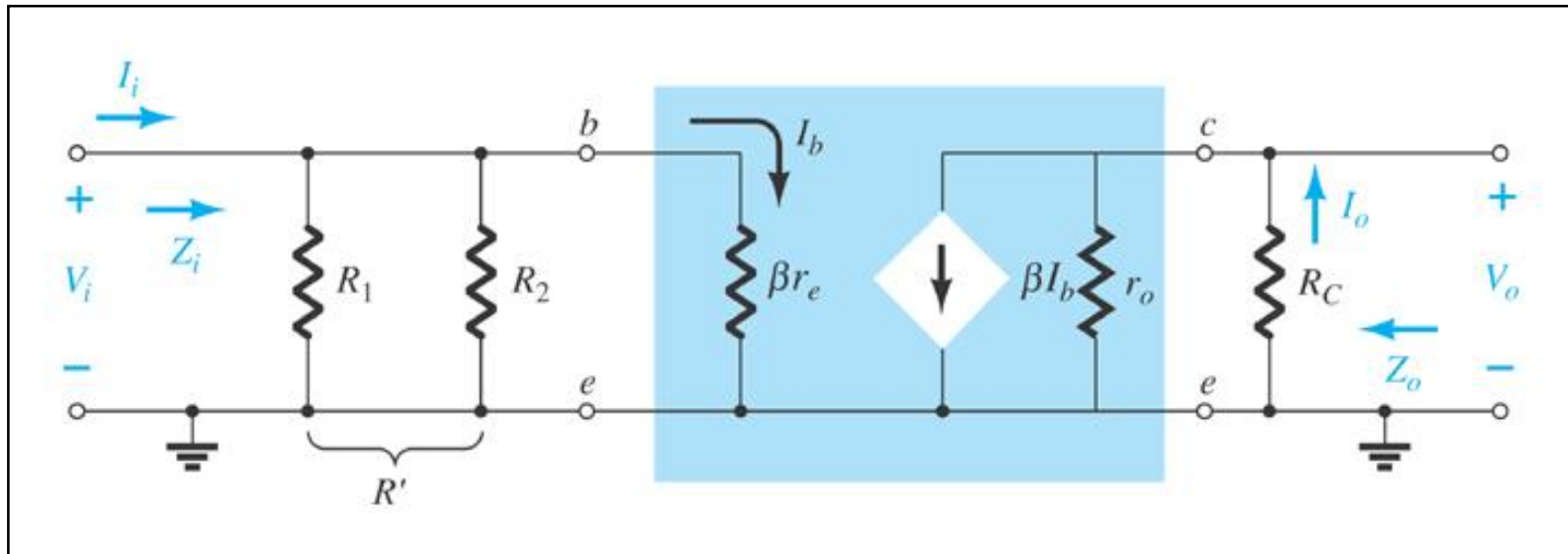

EXAMPLE 5.2 For the network of Fig. 5.28, determine:

- r_e .
- Z_i .
- Z_o ($r_o = \infty \Omega$).
- A_v ($r_o = \infty \Omega$).
- The parameters of parts (b) through (d) if $r_o = 50 \text{ k}\Omega$ and compare results.

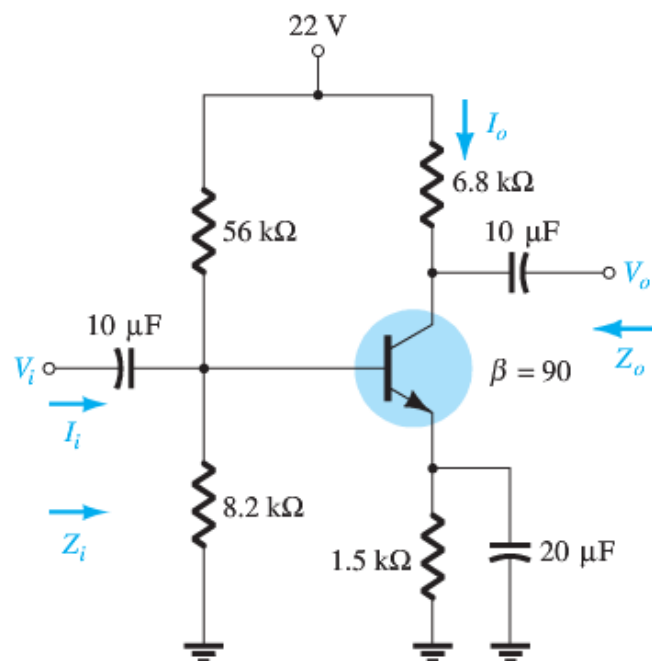


FIG. 5.28
Example 5.2.

Testing $\beta R_E > 10R_2$,

$$(90)(1.5 \text{ k}\Omega) > 10(8.2 \text{ k}\Omega)$$

$$135 \text{ k}\Omega > 82 \text{ k}\Omega \text{ (satisfied)}$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{(8.2 \text{ k}\Omega)(22 \text{ V})}{56 \text{ k}\Omega + 8.2 \text{ k}\Omega} = 2.81 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.81 \text{ V} - 0.7 \text{ V} = 2.11 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{2.11 \text{ V}}{1.5 \text{ k}\Omega} = 1.41 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.41 \text{ mA}} = \mathbf{18.44 \Omega}$$

$$\text{b. } R' = R_1 \parallel R_2 = (56 \text{ k}\Omega) \parallel (8.2 \text{ k}\Omega) = 7.15 \text{ k}\Omega$$

$$Z_i = R' \parallel \beta r_e = 7.15 \text{ k}\Omega \parallel (90)(18.44 \Omega) = 7.15 \text{ k}\Omega \parallel 1.66 \text{ k}\Omega = \mathbf{1.35 \text{ k}\Omega}$$

$$\text{c. } Z_o = R_C = \mathbf{6.8 \text{ k}\Omega}$$


$$\text{d. } A_v = -\frac{R_C}{r_e} = -\frac{6.8 \text{ k}\Omega}{18.44 \Omega} = \mathbf{-368.76}$$

$$\text{e. } Z_i = \mathbf{1.35 \text{ k}\Omega}$$

$$Z_o = R_C \parallel r_o = 6.8 \text{ k}\Omega \parallel 50 \text{ k}\Omega = \mathbf{5.98 \text{ k}\Omega} \text{ vs. } 6.8 \text{ k}\Omega$$

$$A_v = -\frac{R_C \parallel r_o}{r_e} = -\frac{5.98 \text{ k}\Omega}{18.44 \Omega} = \mathbf{-324.3} \text{ vs. } -368.76$$

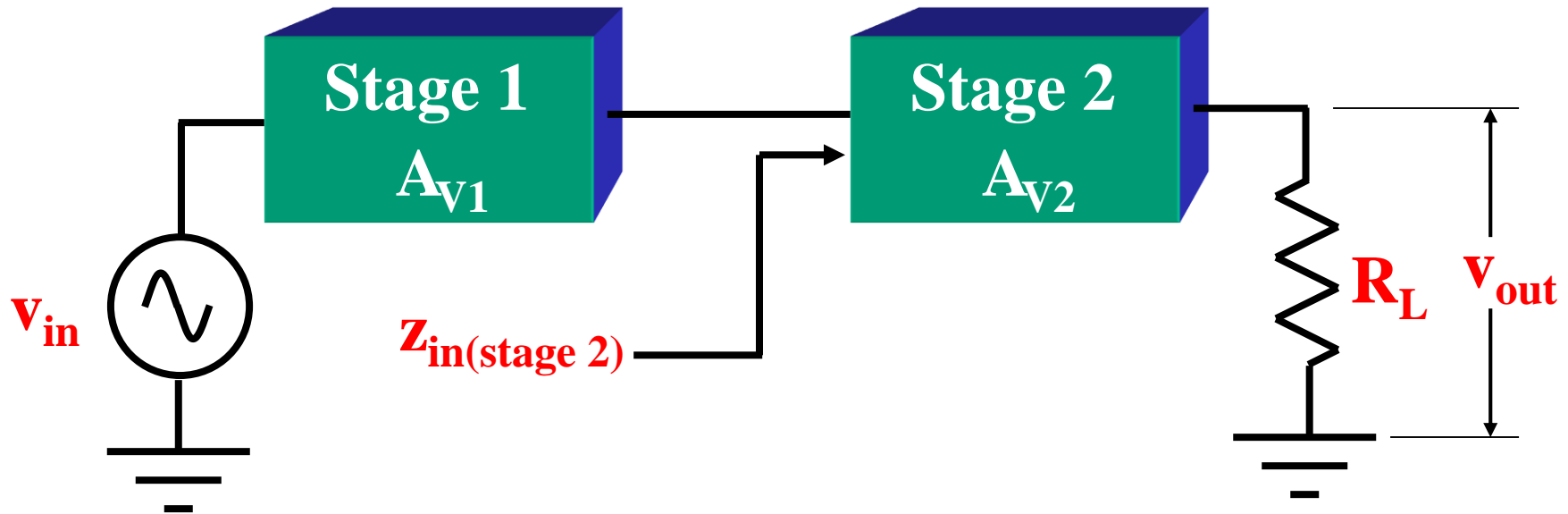To get more gain, a cascaded amplifier can be used.



The overall voltage gain: $A_V = A_{V1}A_{V2}$

- The output of one amplifier is the input to the next amplifier
- The DC bias circuits are isolated from each other by the coupling capacitors

R-C Coupled BJT Amplifiers

Voltage gain:


$$A_{v1} = \frac{R_C \parallel R_1 \parallel R_2 \parallel \beta R_e}{r_e}$$

$$A_{v2} = \frac{R_C}{r_e}$$

$$A_v = A_{v1} A_{v2}$$

Input impedance,
first stage:

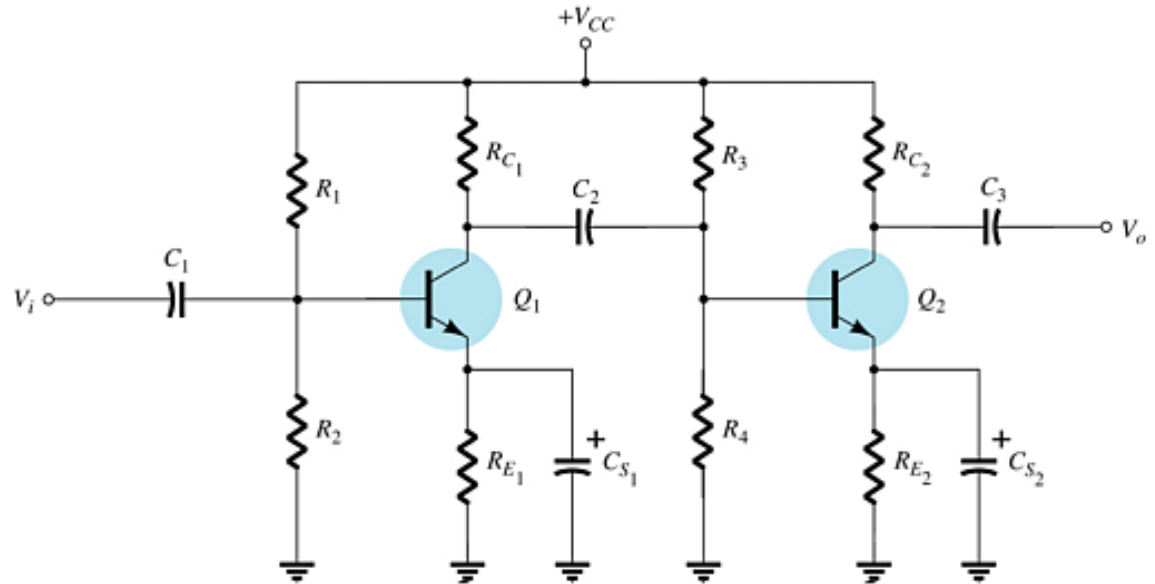
$$Z_i = R_1 \parallel R_2 \parallel \beta R_e$$



Output impedance,
second stage:

$$Z_o = R_C$$

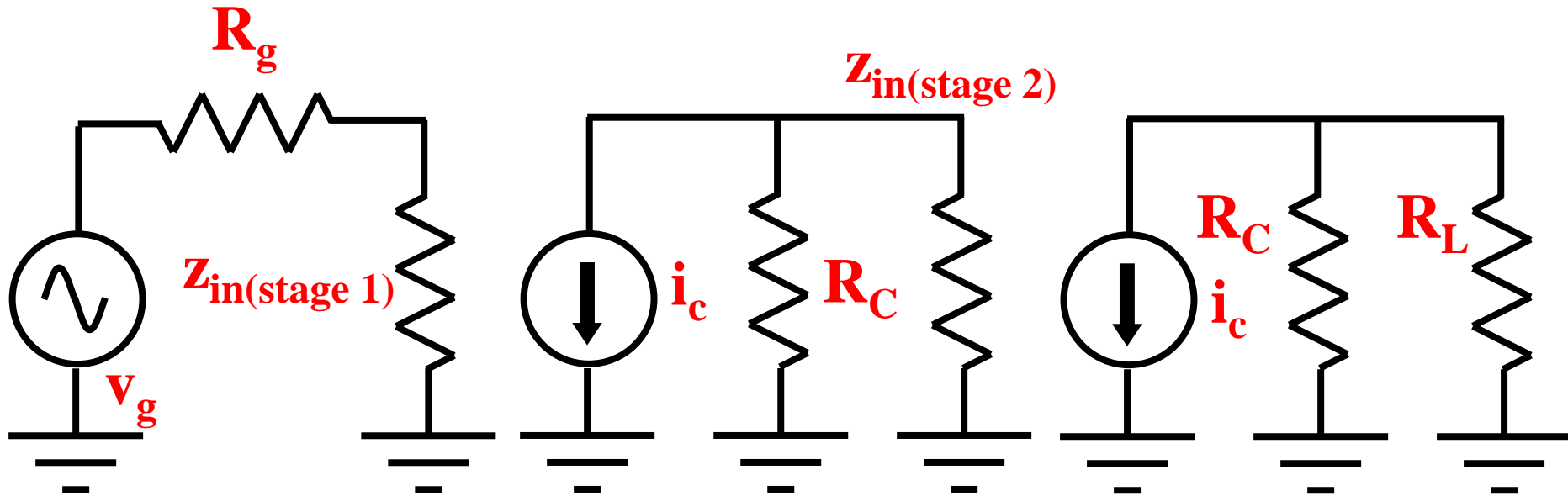Ac equivalent circuit for the two-stage amplifier



The 2nd stage loads the 1st stage:

$$R_{c1} = R_C \parallel Z_{in} \text{ (stage 2)}$$

The Hybrid π Model

The hybrid pi model is most useful for analysis of high-frequency transistor applications.

At lower frequencies the hybrid pi model closely approximate the r_e parameters, and can be replaced by them.

The Hybrid Equivalent Model

Hybrid parameters are developed and used for modeling the transistor. These parameters can be found on a transistor's specification sheet:

h_i = input resistance

h_r = reverse transfer voltage ratio ($V_i/V_o \cong 0$)

h_f = forward transfer current ratio (I_o/I_i)

h_o = output conductance

